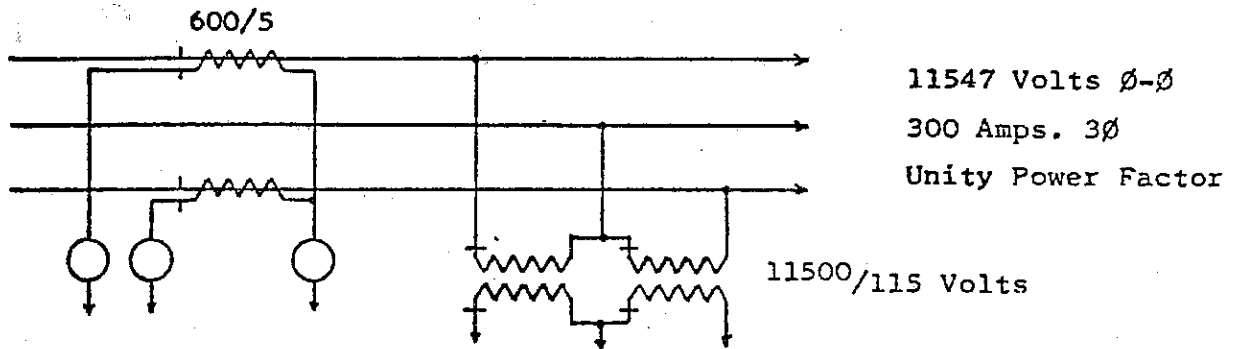


Calculating Meter Multipliers

1. Three wire - three phase using two element wattmeter with two C.T.'s and two P.T.'s



Assume: 11.55KV at 300 Amps., unity power factor


C.T.'s = 600/5 or 120/1, P.T.'s = 100/1

$$\text{Pri. Watts} = 11547 \times 300 \times 1.732$$

$$= 6,000,000 \text{ watts or } 6,000 \text{ KW}$$

$$\text{Sec. Watts} = 115.47 \times 2.5 \times 1.732$$
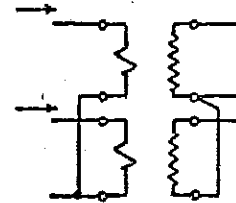
$$= 500 \text{ watts or } 0.5 \text{ KW}$$




Meter must be multiplied by $\frac{\text{Primary watts}}{\text{Secondary watts}}$ to convert meter watts to primary watts

$$\text{Therefore multiplier} = \frac{6,000,000}{500} = 12,000$$

This is identical to the product of C.T. ratio \times P.T. ratio
(120 \times 100) or 12,000

Three wire - two element metering: Multiplier = C.T. \times P.T.

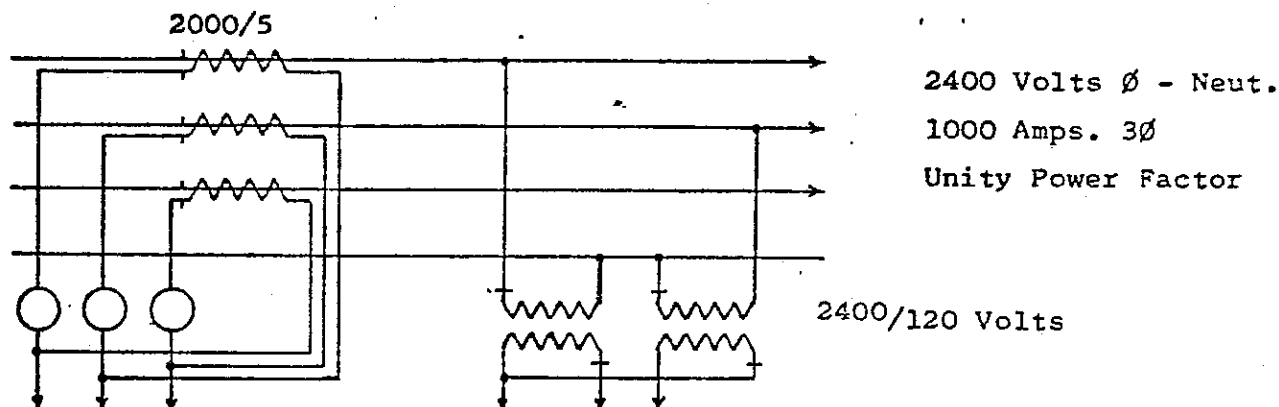2. Four wire - three phase metering using two element wattmeter
three C.T.'s and two P.T.'s connected phase to neutral
(present 4 KV metering)



Assume: 2.4KV Ø to Neutral, 1000 Amps, unity P.F.


C.T.'s = 2000/5 or 400/1, P.T.'s = 20/1

Pri. Watts = $3 \times 2400V_{\phi-N} \times 1000A$

= 7,200,000 watts or 7,200 KW

Sec. Watts = $4.33 \times 120 \times 1.732$

= 900 watts or 0.9 KW

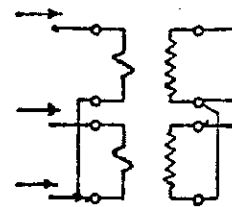


Meter must be multiplied by $\frac{\text{Primary watts}}{\text{Secondary watts}}$ to convert
meter watts to primary watts.

Therefore multiplier = $\frac{7,200,000}{900} = 8,000$

This is identical to the product of C.T. ratio x P.T. ratio
(400 x 20) or 8,000

Four wire - two element metering using three C.T.'s connected
delta and two P.T.'s connected phase to neutral: Multiplier = C.T. x P.T.

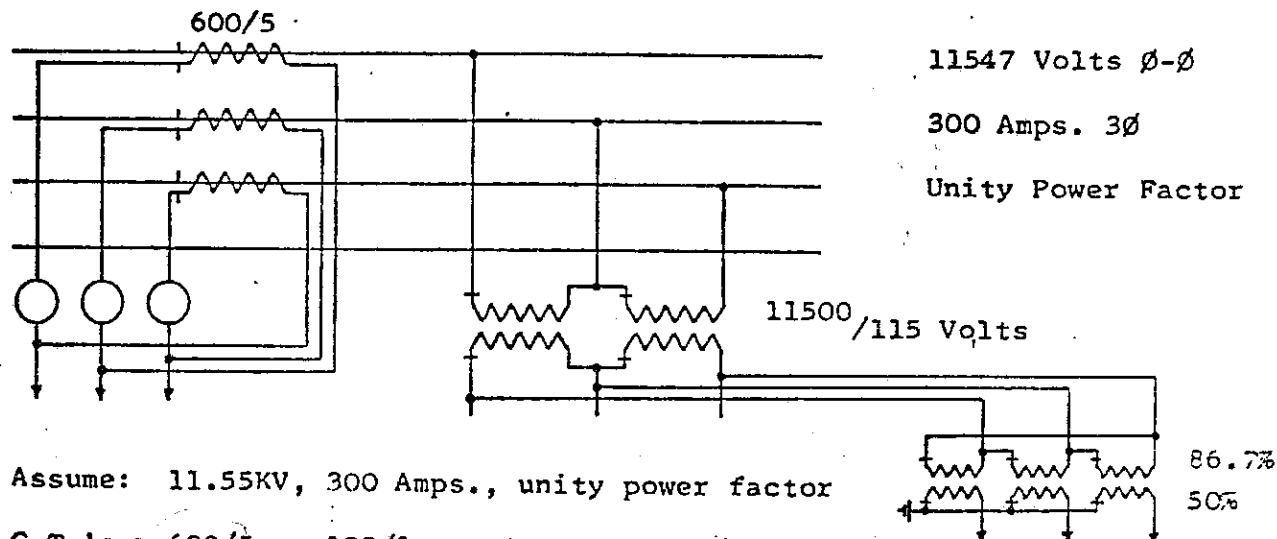3. Four wire - three phase metering using two element wattmeter, three C.T.'s, two P.T.'s connected phase to phase and three auxiliary secondary phase shifting transformers. (present 12KV or 16KV metering)



$$\begin{aligned} \text{Pri. Watts} &= 11547 \times 300 \times 1.732 \\ &= 6,000,000 \text{ watts or } 6,000 \text{ KW} \end{aligned}$$

$$\begin{aligned} \text{Sec. Watts} &= 115.47 \times 4.33 \times 1.732 \\ &= 866 \text{ watts or } 0.866 \text{ KW} \end{aligned}$$


Meter must be multiplied by $\frac{\text{Primary watts}}{\text{Secondary watts}}$ to convert meter watts to primary watts

$$\text{Therefore multiplier} = \frac{6,000,000}{866} = 6928$$

In This case the multiplier is not the product of C.T. ratio \times P.T. ratio ($120 \times 100 = 12,000 \neq 6928$)

Four wire - two element metering using three C.T.'s connected delta, two P.T.'s connected phase to phase and three auxiliary phase shifting transformers: Multiplier = $\frac{\text{C.T.} \times \text{P.T.}}{1.732}$

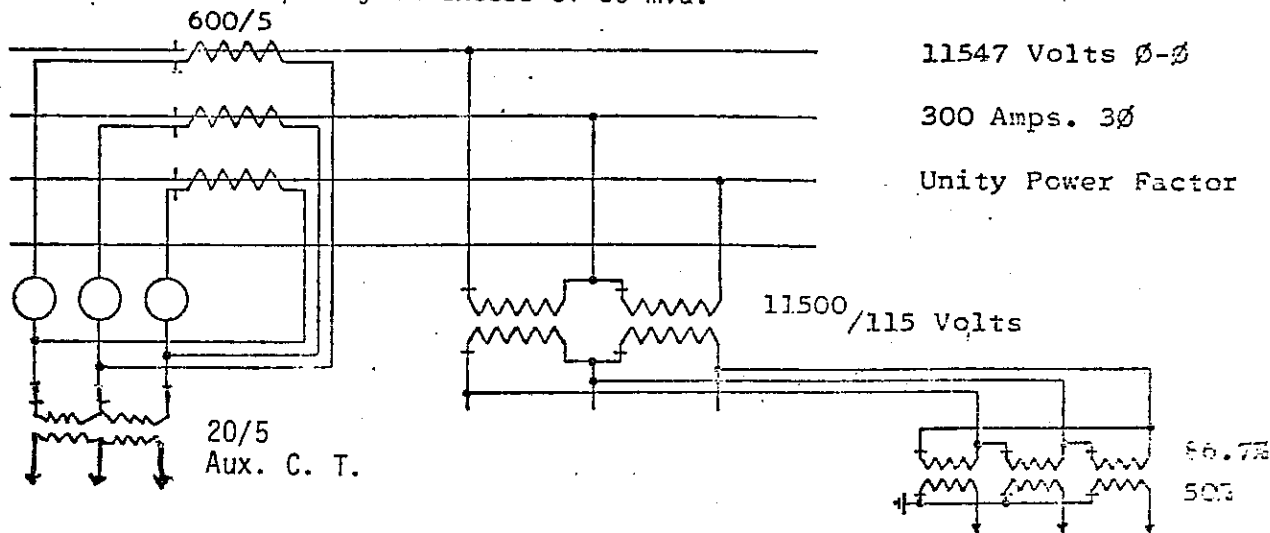4. Four wire - three phase metering using two element wattmeter, three C. T.'s, two P. T.'s connected phase to phase and three auxiliary secondary phase shifting transformers plus two 20/5 auxiliary C. T.'s for station with capacity in excess of 50 mva.




Assume: 11.55 kV, 300 Amps., unity power factor

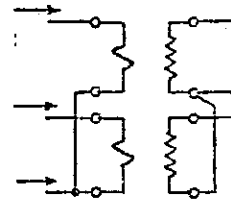C. T.'s = 600/5 or 120/1, P. T.'s = 100/1

$$\begin{aligned} \text{Pri. Watts} &= 11547 \times 300 \times 1.732 \\ &= 6,000,000 \text{ watts or } 6,000 \text{ kw} \end{aligned}$$

$$\begin{aligned} \text{Sec. Watts} &= 115.47 \times 1.0825 \times 1.732 \\ &= 216.5 \text{ watts} \end{aligned}$$



Meter must be multiplied by $\frac{\text{Primary watts}}{\text{Secondary watts}}$ to convert meter watts to primary watts

$$\text{Therefore multiplier} = \frac{6,000,000}{216.5} = 27714$$

In this case the multiplier is not the product of C. T. ratio x P. T. ratio x Aux. C. T. Ratio ($120 \times 100 \times 4 = 48000 \neq 27,714$)

Four wire - two element metering using three C. T.'s connected delta, two P. T.'s connected phase to phase and three auxiliary phase shifting transformers and two auxiliary C. T.'s: Multiplier = $\frac{\text{C. T.} \times \text{P. T.} \times \text{Aux. C. T.}}{1.732}$

DO NOT
CONSIDER
DELTA IN
THE RATIO